 


# CEE 445

## TV Remote Controller and Decoding Technique

Cheng Liu




# How TV Remote Control Works?

- ❖ TV Remote (transmitter and receiver operated between 38K and 56KHz)
  - Consists of an IR LED transmitter and a photo-sensitive detector/receiver (eg. Tsup38238, wavelength at 980nm)
  - Wireless communication (typically at 38KHz)
  - The messages travel via electromagnetic waves just above radio in frequency – the infrared.
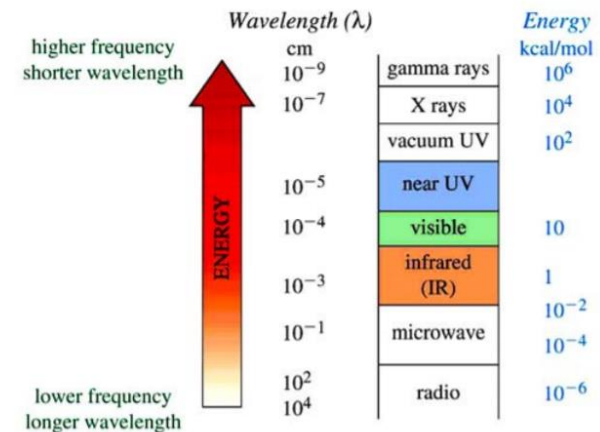
## ❖ How it Works

- The LED transmitter sends a special code assigned to that key as a beam of infrared light pulses.
- The infrared receiver converts it into electrical impulses that correspond to the key code that controls the appliance.



Graphics source: Wade, Jr., Pearson Education Inc., 2003

# Modulation

## ❖ Problem:


- The sun and light bulbs radiate infrared lights at 980 nm. ☹️
- A solution needed for the appliance infrared receiver to differentiate between infrared light sent by the remote control and the infrared light from the sun.

## ❖ Modulation to the rescue


- The appliance infrared receiver is designed to respond not only to infrared light at a frequency of 980nm but also to light that is modulated at a frequency of 38KHz.
- The remote control can ignore signals except the infrared light beam modulated at 38KHz.
 
# NEC IR Protocol



- One of the commonly used IR protocols
- NEC format:
  - 8-bit custom code and 8-bit data code
  - 38KHz - Carrier Frequency
  - Pulse modulation
  - Leader code has 9ms carrier waveform and 4.5ms OFF waveform, followed by a custom code and data code and their inverse.



# IR Decoder

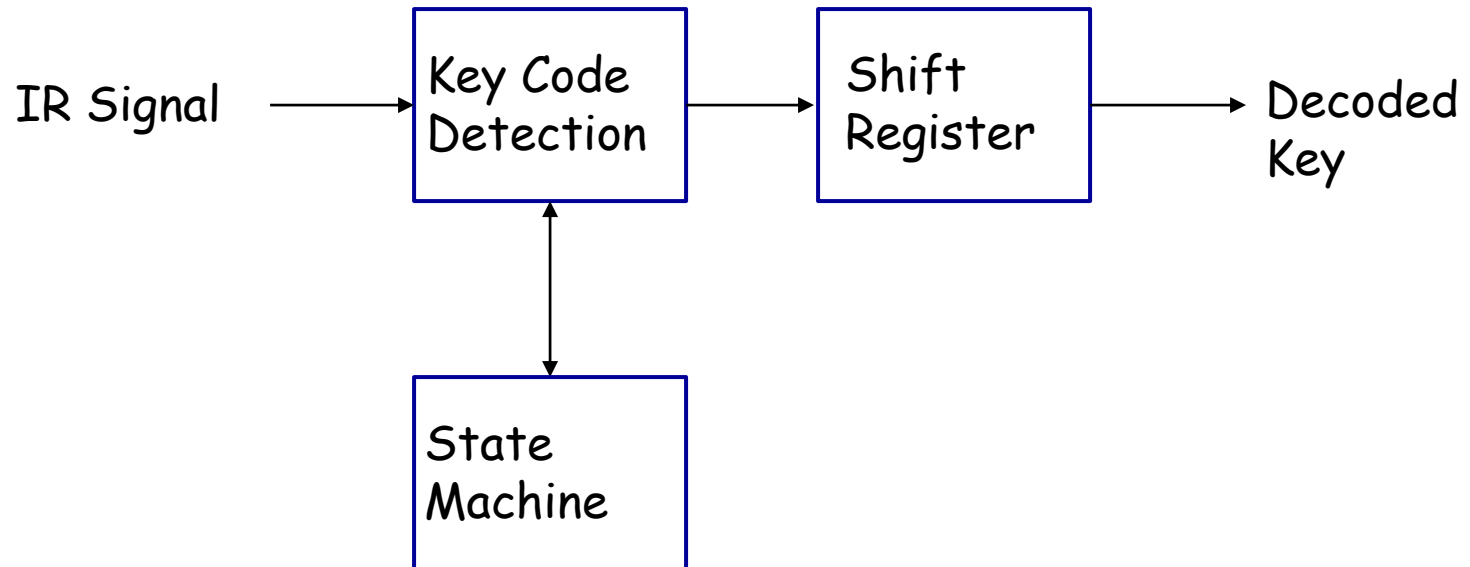

# State Machine

 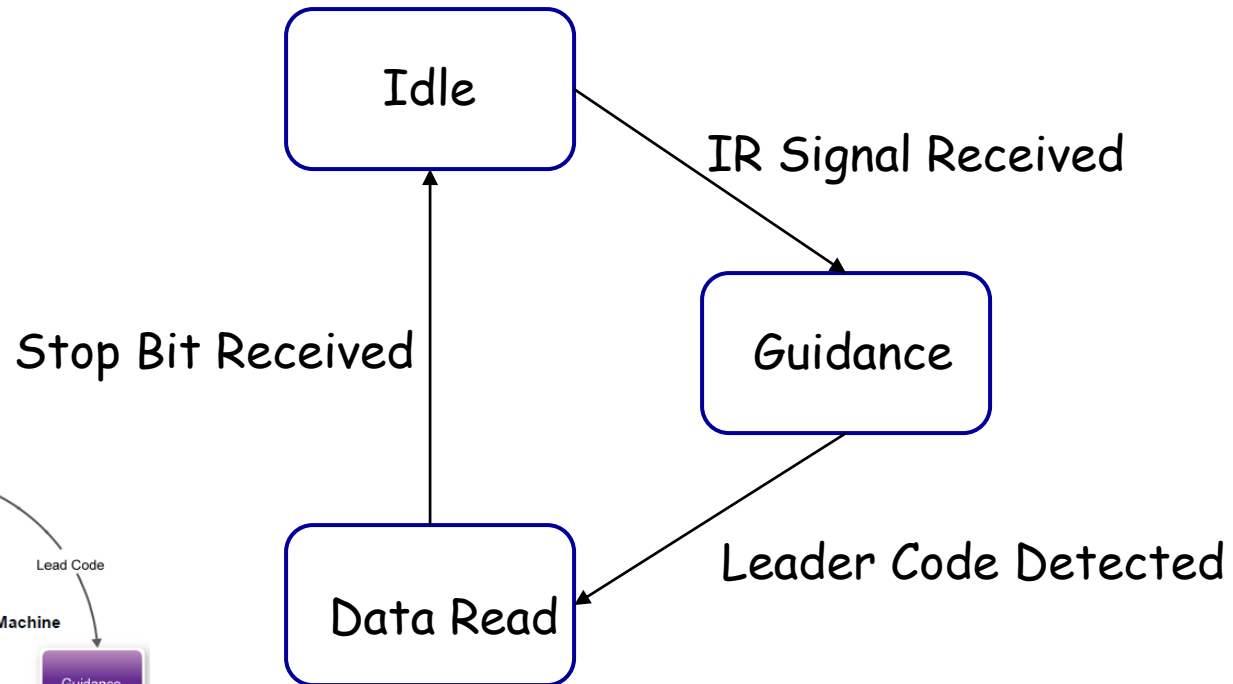

# Lab 8 IR Sensor Interface w/FPGA

# Verilog Model (IR Receiver)

```
module IR_RECEIVE(  
    iCLK,           //clk 50MHz  
    iRST_n,         //reset  
    iIRDA,          //IR code input  
    oDATA_READY,    //data ready  
    oDATA           //decode data output  
);  
  
//=====   
//  PARAMETER declarations   
//=====   
parameter IDLE      = 2'b00; //state Idle: always at a high voltage level  
parameter GUIDANCE  = 2'b01; //state guidance; 9ms at a low voltage and 4.5 ms at a high voltage  
parameter DATAREAD   = 2'b10; //state; read IR data  
  
parameter IDLE_HIGH_DUR = 262143; // data_count    262143*0.02us = 5.24ms, threshold for DATAREAD-----> IDLE  
parameter GUIDE_LOW_DUR  = 230000; // idle_count    230000*0.02us = 4.60ms, threshold for IDLE----->GUIDANCE  
parameter GUIDE_HIGH_DUR = 210000; // state_count   210000*0.02us = 4.20ms, 4.5-4.2 = 0.3ms < BIT_AVAILABLE_DUR =  
                                // 0.4ms,threshold for GUIDANCE----->DATAREAD  
parameter DATA_HIGH_DUR = 41500;  // data_count    41500 *0.02us = 0.83ms, sample time from the posedge of iIRDA  
parameter BIT_AVAILABLE_DUR = 20000; // data_count    20000 *0.02us = 0.4ms, the sample bit  
                                // pointer,can inhibit the interference from iIRDA signal
```



# Verilog Model (IR Receiver)

```
//=====
//  PORT declarations
//=====
input      iCLK;          //input clk,50MHz
input      iRST_n;        //rst
input      iIRDA;         //Irda RX output decoded data
output     oDATA_READY;   //data ready
output [31:0] oDATA;       //output data,32bit

//=====
//  Signal Declarations
//=====
reg [31:0] oDATA;          //data output reg
reg [17:0] idle_count;     //idle counter; run in the data_read state
reg        idle_count_flag; //idle_count conter flag
reg [17:0] state_count;    //state_count; run in guidance state
reg        state_count_flag; //state_count conter flag
reg [17:0] data_count;     //data_count; run in data_read state
reg        data_count_flag; //data_count conter flag
reg [5:0] bitcount;        //sample bit pointer
reg [1:0] state;           //state reg
reg [31:0] data;           //data reg
reg [31:0] data_buf;       //data buf
reg        data_ready;     //data ready flag
```

# Verilog Model (IR Receiver)

```
//=====
//  Structural coding
//=====
assign oDATA_READY = data_ready;

//idle counter runs at IDLE state only
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        idle_count <= 0;
    else if (idle_count_flag) //the counter runs when the flag is 1
        idle_count <= idle_count + 1'b1;
    else
        idle_count <= 0; //the counter resets when the flag is 0

//idle counter job complete when iIRDA is low in the IDLE state
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        idle_count_flag <= 1'b0;
    else if ((state == IDLE) && !iIRDA)
        idle_count_flag <= 1'b1;
    else
        idle_count_flag <= 1'b0;
```

Idle count is to measure the IR LED "ON" time during the IDLE state

Idle count flag indicates IR LED "ON" time ends and the counter job and IR LED returns To LOW state.

# Verilog Model (IR Receiver)

```
//state counter runs in the GUIDANCE state only
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        state_count <= 0;
    else if (state_count_flag) //the counter runs when the flag is 1
        state_count <= state_count + 1'b1;
    else
        state_count <= 0; //the counter resets when the flag is 0

//state counter job complete when iIRDA is high in the GUIDANCE state
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        state_count_flag <= 1'b0;
    else if ((state == GUIDANCE) && iIRDA)
        state_count_flag <= 1'b1;
    else
        state_count_flag <= 1'b0;
```

State count is to measure "OFF" time of the IR LED during the GUIDANCE state

State count flag is to detect if the IR LED Changes from "ON" to "OFF"

# Verilog Model (IR Receiver)

```
//data read counter runs on iCLK clock
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        data_count <= 1'b0;
    else if(data_count_flag)           //the counter runs when the flag is 1
        data_count <= data_count + 1'b1;
    else
        data_count <= 1'b0;           //the counter resets when the flag is 0

//data counter job complete
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        data_count_flag <= 0;
    else if ((state == DATAREAD) && iIRDA)
        data_count_flag <= 1'b1;
    else
        data_count_flag <= 1'b0;
```

Data count variable detects if IR data is '1' or '0'. This counter increments when a logic '1' is received.

Data count flag detects if IR LED changes from "ON" to "OFF"

# Verilog Model

Data reg. pointer counter  
determines how many data bit to  
read in the Data Read state.

## State Machine

```
//data reg pointer counter
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        bitcount <= 6'b0;
    else if (state == DATAREAD)
        begin
            if (data_count == 20000)
                bitcount <= bitcount + 1'b1; //add 1 when iIRDA posedge
        end
    else
        bitcount <= 6'b0;

//state change between IDLE,GUIDE,DATA_READ according to irda edge or counter value
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        state <= IDLE;
    else
        case (state)
            IDLE      : if (idle_count > GUIDE_LOW_DUR) // state chang from IDLE to Guidance when detect the negedge
                                                                //and the low voltage last for > 4.6ms
                            state <= GUIDANCE;
            GUIDANCE  : if (state_count > GUIDE_HIGH_DUR) //state change from GUIDANCE to DATAREAD when detect
                                                                //the posedge and the high voltage last for > 4.2ms
                            state <= DATAREAD;
            DATAREAD  : if ((data_count >= IDLE_HIGH_DUR) || (bitcount >= 33))
                            state <= IDLE;
            default   : state <= IDLE; //default
        endcase
```

# Verilog Model (IR Receiver)

```
//data decoding
always @(posedge iCLK or negedge iRST_n)
  if (!iRST_n)
    data <= 0;
  else if (state == DATAREAD)
    begin
      if (data_count >= DATA_HIGH_DUR) //2^15 = 32767*0.02us = 0.64us
        data[bitcount-1'b1] <= 1'b1; //>0.52ms sample the bit 1
      end
    else
      data <= 0;
```

Shift register - storing the IR data into a data array.

```
//set the data_ready flag
always @(posedge iCLK or negedge iRST_n)
  if (!iRST_n)
    data_ready <= 1'b0;
  else if (bitcount == 32)
    begin
      if (data[31:24] == ~data[23:16])
        begin
          data_buf <= data; //fetch the value to the databuf from the data reg
          data_ready <= 1'b1; //set the data ready flag
        end
      else
        data_ready <= 1'b0 ; //data error
    end
  else
    data_ready <= 1'b0 ;
```

Data ready is set and IR data is stored in a data array only if the IR code matches with a key press on the remote control.

# Verilog Model (IR Receiver)

```
//read data
always @(posedge iCLK or negedge iRST_n)
    if (!iRST_n)
        oDATA <= 32'b00000;
    else if (data_ready)
        oDATA <= data_buf; //output
endmodule
```

The oData variable contains  
a valid IR code

# Verilog Model (7-Seg Display)

A valid IR code is then displayed on a 7-seg. display

```
module SEG_HEX
(
    ////////////////////////////////////////////////// 4 Binary bits Input
    iDIG,
    ////////////////////////////////////////////////// HEX 7-SEG Output
    oHEX_D
);

////////////////////////////////////////////////// Binary bis Input
input  [3:0] iDIG;
////////////////////////////////////////////////// HEX 7-SEG Output
output [6:0] oHEX_D;


reg [6:0] oHEX_D;
```

```
//=====
// Structural coding
//=====
always @(iDIG)
begin
    case(iDIG)
        4'h0: oHEX_D <= 7'b1000000; //0
        4'h1: oHEX_D <= 7'b1111001; //1
        4'h2: oHEX_D <= 7'b0100100; //2
        4'h3: oHEX_D <= 7'b0110000; //3
        4'h4: oHEX_D <= 7'b0011001; //4
        4'h5: oHEX_D <= 7'b0010010; //5
        4'h6: oHEX_D <= 7'b0000010; //6
        4'h7: oHEX_D <= 7'b1111000; //7
        4'h8: oHEX_D <= 7'b0000000; //8
        4'h9: oHEX_D <= 7'b0011000; //9
        4'ha: oHEX_D <= 7'b0001000; //a
        4'hb: oHEX_D <= 7'b0000011; //b
        4'hc: oHEX_D <= 7'b1000110; //c
        4'hd: oHEX_D <= 7'b0100001; //d
        4'he: oHEX_D <= 7'b0000110; //e
        4'hf: oHEX_D <= 7'b0001110; //f
        default: oHEX_D <= 7'b1000000; //0
    endcase
end

endmodule
```



# Demo

 

Remote  
Controller



Custom Code    Key Code

IR  
Receiver

Key code information for each Key on remote controller

Key	Key Code	Key	Key Code	Key	Key Code	Key	Key Code
	0x0F		0x13		0x10		0x12
	0x01		0x02		0x03		0x1A
	0x04		0x05		0x06		0x1E
	0x07		0x08		0x09		0x1B
	0x11		0x00		0x17		0x1F
	0x16		0x14		0x18		0x0C

